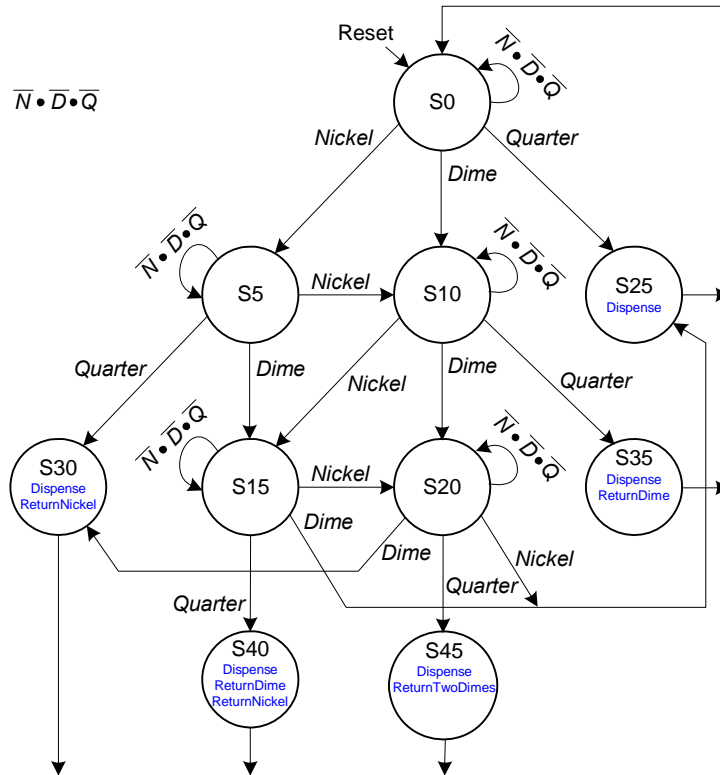


Exercise 3.26



Note: $\overline{N} \cdot \overline{D} \cdot \overline{Q} = \overline{\text{Nickel}} \cdot \overline{\text{Dime}} \cdot \overline{\text{Quarter}}$

FIGURE 3.2 State transition diagram for soda machine dispense of Exercise 3.23

state	encoding $s_{9:0}$
S0	000000001
S5	000000010
S10	000000100
S25	000001000
S30	000010000
S15	000100000
S20	000100000
S35	001000000
S40	010000000
S45	100000000

FIGURE 3.3 State Encodings for Exercise 3.26

current state s	inputs			next state s'
	<i>nickel</i>	<i>dime</i>	<i>quarter</i>	
S0	0	0	0	S0
S0	0	0	1	S25
S0	0	1	0	S10
S0	1	0	0	S5
S5	0	0	0	S5
S5	0	0	1	S30
S5	0	1	0	S15
S5	1	0	0	S10
S10	0	0	0	S10

TABLE 3.11 State transition table for Exercise 3.26

current state s	inputs			next state s'
	<i>nickel</i>	<i>dime</i>	<i>quarter</i>	
S10	0	0	1	S35
S10	0	1	0	S20
S10	1	0	0	S15
S25	X	X	X	S0
S30	X	X	X	S0
S15	0	0	0	S15
S15	0	0	1	S40
S15	0	1	0	S25
S15	1	0	0	S20
S20	0	0	0	S20
S20	0	0	1	S45
S20	0	1	0	S30
S20	1	0	0	S25
S35	X	X	X	S0
S40	X	X	X	S0
S45	X	X	X	S0

TABLE 3.11 State transition table for Exercise 3.26

current state s	inputs			next state s'
	<i>nickel</i>	<i>dime</i>	<i>quarter</i>	
000000001	0	0	0	000000001
000000001	0	0	1	000001000
000000001	0	1	0	000000100
000000001	1	0	0	000000010

TABLE 3.12 State transition table for Exercise 3.26

current state <i>s</i>	inputs			next state <i>s'</i>
	<i>nickel</i>	<i>dime</i>	<i>quarter</i>	
000000010	0	0	0	000000010
000000010	0	0	1	000010000
000000010	0	1	0	000010000
000000010	1	0	0	000000100
000000100	0	0	0	000000100
000000100	0	0	1	001000000
000000100	0	1	0	000100000
000000100	1	0	0	000010000
000001000	X	X	X	000000001
000001000	X	X	X	000000001
000010000	0	0	0	000010000
000010000	0	0	1	010000000
000010000	0	1	0	000001000
000010000	1	0	0	000100000
000100000	0	0	0	000100000
000100000	0	0	1	100000000
000100000	0	1	0	000001000
000100000	1	0	0	000001000
001000000	X	X	X	000000001
010000000	X	X	X	000000001
100000000	X	X	X	000000001

TABLE 3.12 State transition table for Exercise 3.26

$$s_9 = s_6Q$$

$$s_8 = s_5Q$$

$$S'_7 = S_2Q$$

$$S'_6 = S_2D + S_5N + S_6\overline{NDQ}$$

$$S'_5 = S_1D + S_2N + S_5NDQ$$

$$S'_4 = S_1Q + S_6D$$

$$S'_3 = S_0Q + S_5D + S_6N$$

$$S'_2 = S_0D + S_1N + S_2\overline{NDQ}$$

$$S'_1 = S_0N + S_1NDQ$$


$$S'_0 = S_0\overline{NDQ} + S_3 + S_4 + S_7 + S_8 + S_9$$

$$Dispense = S_3 + S_4 + S_7 + S_8 + S_9$$

$$ReturnNickel = S_4 + S_8$$

$$ReturnDime = S_7 + S_8$$

$$ReturnTwoDimes = S_9$$

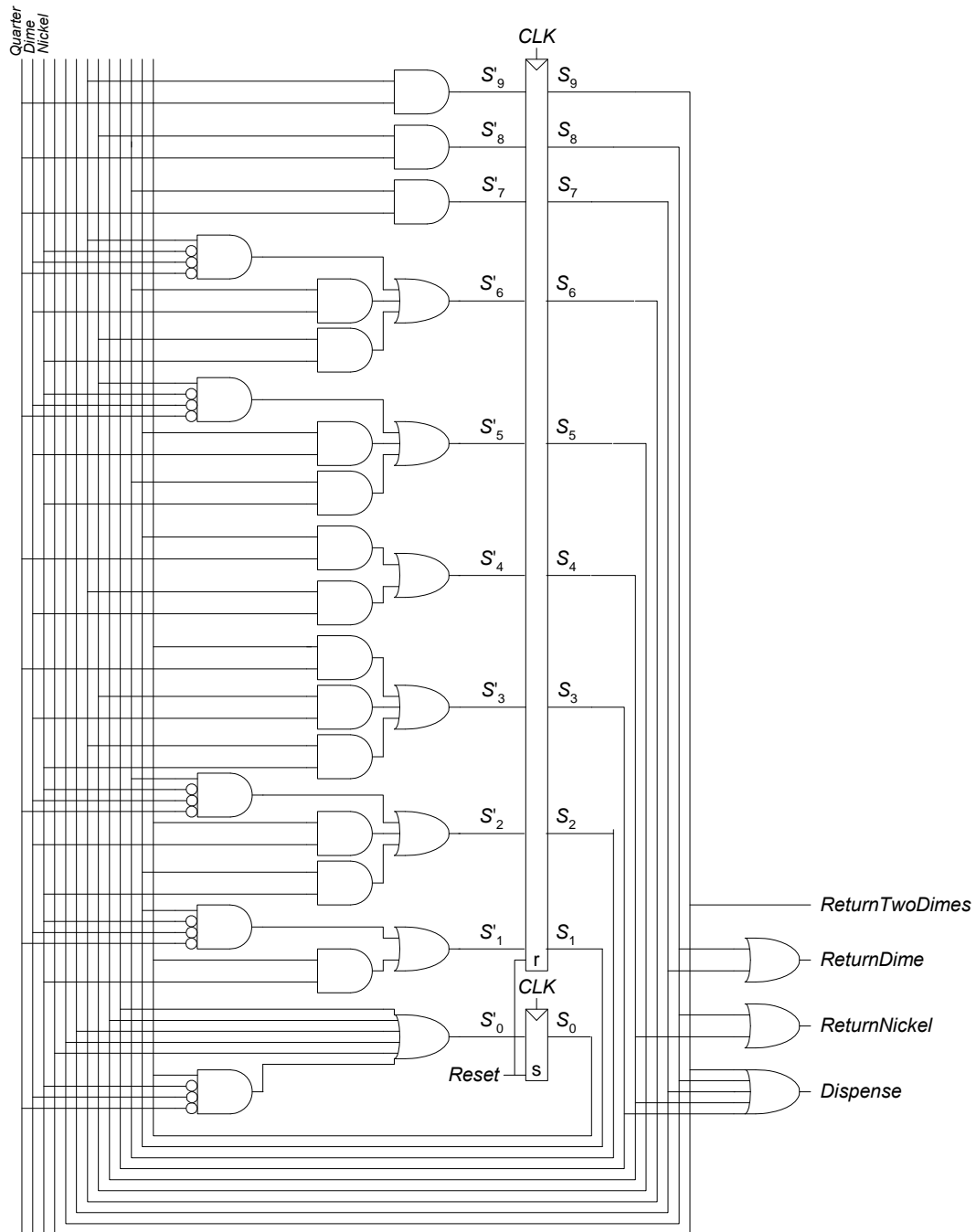

Exercise 3.27

 


FIGURE 3.4 State transition diagram for Exercise 3.27

current state $s_{2:0}$	next state $s'_{2:0}$
000	001
001	011
011	010
010	110
110	111
111	101
101	100
100	000

TABLE 3.13 State transition table for Exercise 3.27

$$S'_2 = S_1\overline{S_0} + S_2S_0$$

$$S'_1 = \overline{S_2}S_0 + S_1\overline{S_0}$$

$$S'_0 = \overline{S_2} \oplus S_1$$

$$Q_2 = S_2$$

$$Q_1 = S_1$$

$$Q_0 = S_0$$

 


FIGURE 3.5 Hardware for Gray code counter FSM for Exercise 3.27

Exercise 3.28

 


FIGURE 3.6 State transition diagram for Exercise 3.28

current state $s_{2:0}$	input up	next state $s'_{2:0}$
000	1	001
001	1	011
011	1	010
010	1	110
110	1	111
111	1	101
101	1	100
100	1	000
000	0	100
001	0	000
011	0	001
010	0	011
110	0	010
111	0	110
101	0	111
100	0	101

TABLE 3.14 State transition table for Exercise 3.28

$$S'_2 = UPS_1\bar{S}_0 + \overline{UP}\bar{S}_1\bar{S}_0 + S_2S_0$$

$$S'_1 = S_1\bar{S}_0 + UP\bar{S}_2S_0 + \overline{UP}S_2S_1$$

$$S'_0 = UP \oplus S_2 \oplus S_1$$

$$Q_2 = S_2$$

$$Q_1 = S_1$$

$$Q_0 = S_0$$

 


FIGURE 3.7 Finite state machine hardware for Exercise 3.28

 
Exercise 3.29

FIGURE 3.8 Waveform showing Z output for Exercise 3.29

(b) This FSM is a Mealy FSM because the output depends on the current value of the input as well as the current state.

(c)

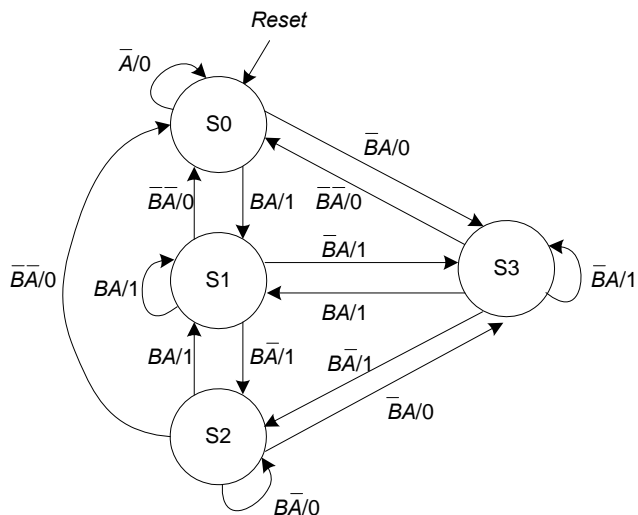


FIGURE 3.9 State transition diagram for Exercise 3.29

(Note: another viable solution would be to allow the state to transition from S0 to S1 on $\bar{B}\bar{A}/0$. The arrow from S0 to S0 would then be $\bar{B}\bar{A}/0$.)

current state $s_{1:0}$	inputs		next state $s'_{1:0}$	output z
	b	a		
00	X	0	00	0
00	0	1	11	0
00	1	1	01	1
01	0	0	00	0
01	0	1	11	1
01	1	0	10	1
01	1	1	01	1
10	0	X	00	0
10	1	0	10	0

TABLE 3.15 State transition table for Exercise 3.29

current state $s_{1:0}$	inputs		next state $s'_{1:0}$	output z
	b	a		
10	1	1	01	1
11	0	0	00	0
11	0	1	11	1
11	1	0	10	1
11	1	1	01	1

TABLE 3.15 State transition table for Exercise 3.29

$$S'_1 = \bar{B}A(\bar{S}_1 + S_0) + B\bar{A}(S_1 + \bar{S}_0)$$

$$S'_0 = A(\bar{S}_1 + S_0 + B)$$

$$Z = BA + S_0(A + B)$$

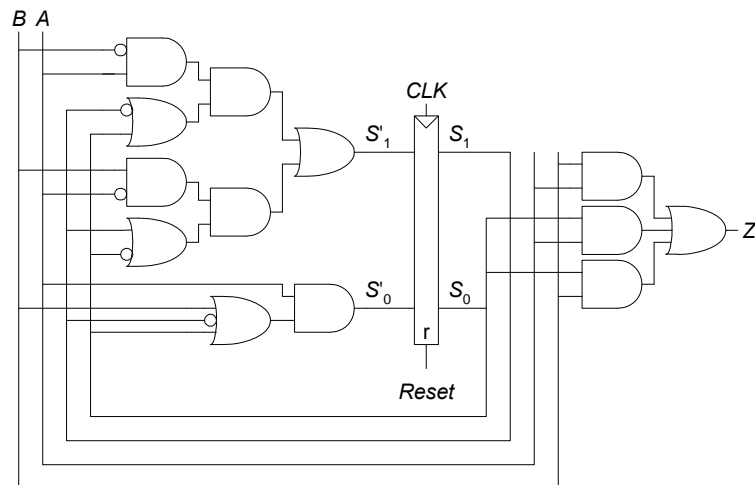


FIGURE 3.10 Hardware for FSM of Exercise 3.26

Note: One could also build this functionality by registering input A , producing both the logical AND and OR of input A and its previous (registered)

value, and then muxing the two operations using B . The output of the mux is Z : $Z = A\bar{A}_{prev}$ (if $B = 0$); $Z = A + A_{prev}$ (if $B = 1$).

Exercise 3.30

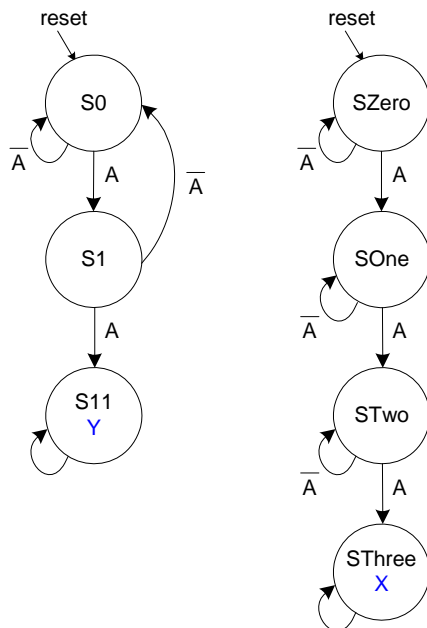


FIGURE 3.11 Factored state transition diagram for Exercise 3.30

current state $s_{1:0}$	input a	next state $s'_{1:0}$
00	0	00
00	1	01
01	0	00

TABLE 3.16 State transition table for output Y for Exercise 3.30

current state $s_{1:0}$	input a	next state $s'_{1:0}$
01	1	11
11	X	11

TABLE 3.16 State transition table for output Y for Exercise 3.30

current state $t_{1:0}$	input a	next state $t'_{1:0}$
00	0	00
00	1	01
01	0	01
01	1	10
10	0	10
10	1	11
11	X	11

TABLE 3.17 State transition table for output X for Exercise 3.30

$$S_1 = S_0(S_1 + A)$$

$$S_0 = \bar{S}_1 A + S_0(S_1 + A)$$

$$Y = S_1$$

$$T_1 = T_1 + T_0 A$$

$$T_0 = A(T_1 + \bar{T}_0) + \bar{A}T_0 + T_1 T_0$$

$$X = T_1 T_0$$

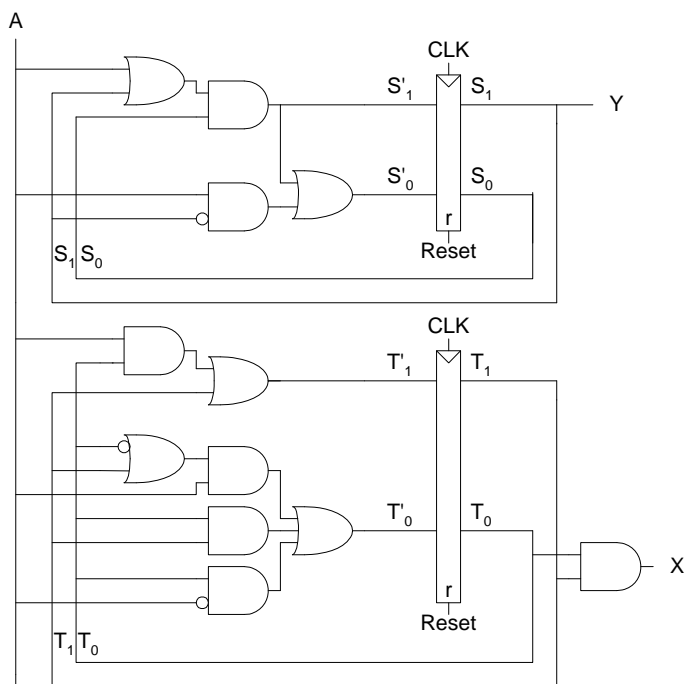


FIGURE 3.12 Finite state machine hardware for Exercise 3.30

Exercise 3.31

This finite state machine is a divide-by-two counter (see Section 3.4.2) when $X = 0$. When $X = 1$, the output, Q , is HIGH.

current state		input	next state	
s_1	s_0	x	s'_1	s'_0
0	0	0	0	1
0	0	1	1	1
0	1	0	0	0


TABLE 3.18 State transition table with binary encodings for Exercise 3.31

current state		input	next state	
s_1	s_0	x	s'_1	s'_0
0	1	1	1	0
1	X	X	0	1

TABLE 3.18 State transition table with binary encodings for Exercise 3.31

current state		output
s_1	s_0	q
0	0	0
0	1	1
1	X	1

TABLE 3.19 Output table for Exercise 3.31

 **Exercise 3.32**

current state			input	next state		
s_2	s_1	s_0	a	s'_2	s'_1	s'_0
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	0	1

TABLE 3.20 State transition table with binary encodings for Exercise 3.32

current state			input	next state		
s_2	s_1	s_0	a	s'_2	s'_1	s'_0
0	1	0	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	1	0	0

TABLE 3.20 State transition table with binary encodings for Exercise 3.32

 


FIGURE 3.13 State transition diagram for Exercise 3.32

Q asserts whenever A is HIGH for two or more consecutive cycles.

Exercise 3.33

(a) First, we calculate the propagation delay through the combinational logic:

$$\begin{aligned}
 t_{pd} &= 3t_{pd_XOR} \\
 &= 3 \times 100 \text{ ps} \\
 &= \mathbf{300 \text{ ps}}
 \end{aligned}$$

Next, we calculate the cycle time:

$$\begin{aligned}
 T_c &\geq t_{pcq} + t_{pd} + t_{setup} \\
 &\geq [70 + 300 + 60] \text{ ps} \\
 &= 430 \text{ ps} \\
 f &= 1 / 430 \text{ ps} = \mathbf{2.33 \text{ GHz}}
 \end{aligned}$$

(b)

$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$


Thus,

$$\begin{aligned}
 t_{skew} &\leq T_c - (t_{pcq} + t_{pd} + t_{setup}), \text{ where } T_c = 1 / 2 \text{ GHz} = 500 \text{ ps} \\
 &\leq [500 - 430] \text{ ps} = \mathbf{70 \text{ ps}}
 \end{aligned}$$

(c)

Exercise 8.13

(a)

 

(b) Each tag is 16 bits. There are 32Kwords / (2 words / block) = 16K blocks and each block needs a tag: $16 \times 16K = 256K = \mathbf{256\ Kbits}$ of tags.

(c) Each cache block requires: 2 status bits, 16 bits of tag, and 64 data bits, thus each set is $2 \times 82 \text{ bits} = \mathbf{164\ bits}$.

(d) See figure below. The design must use enough RAM chips to handle both the total capacity and the number of bits that must be read on each cycle. For the data, the SRAM must provide a capacity of 128 KB and must read 64 bits per cycle (one 32-bit word from each way). Thus the design needs at least $128KB / (8KB/RAM) = 16$ RAMs to hold the data and $64 \text{ bits} / (4 \text{ pins}/RAM) = 16$ RAMs to supply the number of bits. These are equal, so the design needs exactly 16 RAMs for the data.

For the tags, the total capacity is 32 KB, from which 32 bits (two 16-bit tags) must be read each cycle. Therefore, only 4 RAMs are necessary to meet the capacity, but 8 RAMs are needed to supply 32 bits per cycle. Therefore, the design will need 8 RAMs, each of which is being used at half capacity.

With 8K sets, the status bits require another $8K \times 4\text{-bit}$ RAM. We use a $16K \times 4\text{-bit}$ RAM, using only half of the entries.